

Homework #1 ECE 461 / 661


Ladder Logic. Due Monday, August 27th

1) Write a Ladder Logic program to implement the following logic function: $Y = f(A, B, C, D)$

		CD			
		00	01	11	10
AB	00	1	0	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	1	0

$$Y = B'CD' + CD + BD + AD$$

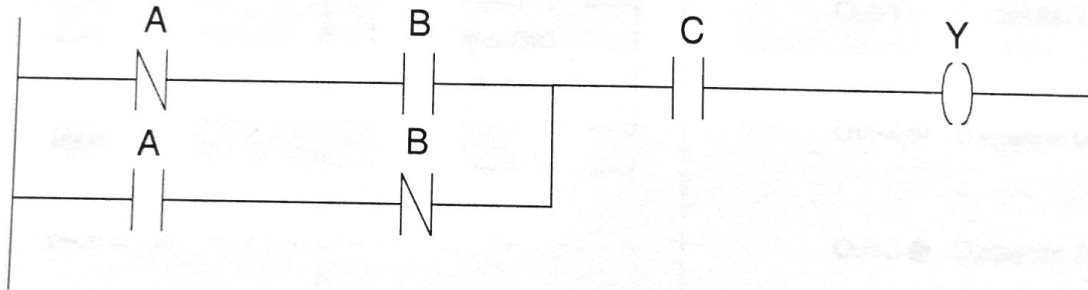2) Determine the logic function which corresponds to the following ladder logic program:



$$Y = (A'B + AB)CC$$

3) Write a ladder logic program to meet the following requirements:

I/O:

- Input: Button 1, 2, 3, 4
- Output: 1 (red) and 3 (green)

How they relate:

- If no buttons are pressed, both lights are off. Otherwise,
- If an even number of buttons are pressed, the red light turns on and the green light is off.
- If an odd number of buttons are pressed, the green light is on and the red light is off.

$$R = 12 + 13 + 14 + 23 + 24 + 34 + 1234$$

others

$$G = 12'34' + 21'3'4' + 31'2'4' + 41'2'3' + 1234' + 123'4 + 12'34 + 1'234$$